

## Lab 4: Arithmetic Logic Unit

Date: 23.10.2023

Name: Şevval ERBAY

Section: 2

### Purpose of the experiment:

The purpose of this lab is to design an arithmetic logic unit (ALU) capable of performing at least eight different operations including addition, subtraction, one bitwise and one shift operation by using VHDL. The VHDL code is implemented in modular fashion.

### Methodology:

The selected operations are: addition, subtraction, bitwise OR-gate, bitwise AND-gate, pass through, ones' complement, left logical shift and right logical shift. A half-adder and a full-adder is created to use in the addition and subtraction operations. Main module alu.vhd has the other operations in a modular fashion. 2 different 4-bit signed numbers, **a** and **b**, 3-bit select option **sel**, 4-bit output **out0** and a carry **car** are used in the operations. RTL schematic is created, and a test bench is written to check whether the operations are working properly or not. In order to be sure, another test bench is utilized. Lastly, the constraint code is written and bit stream is generated. The process is simulated by using BASYS3's switches and LEDs.


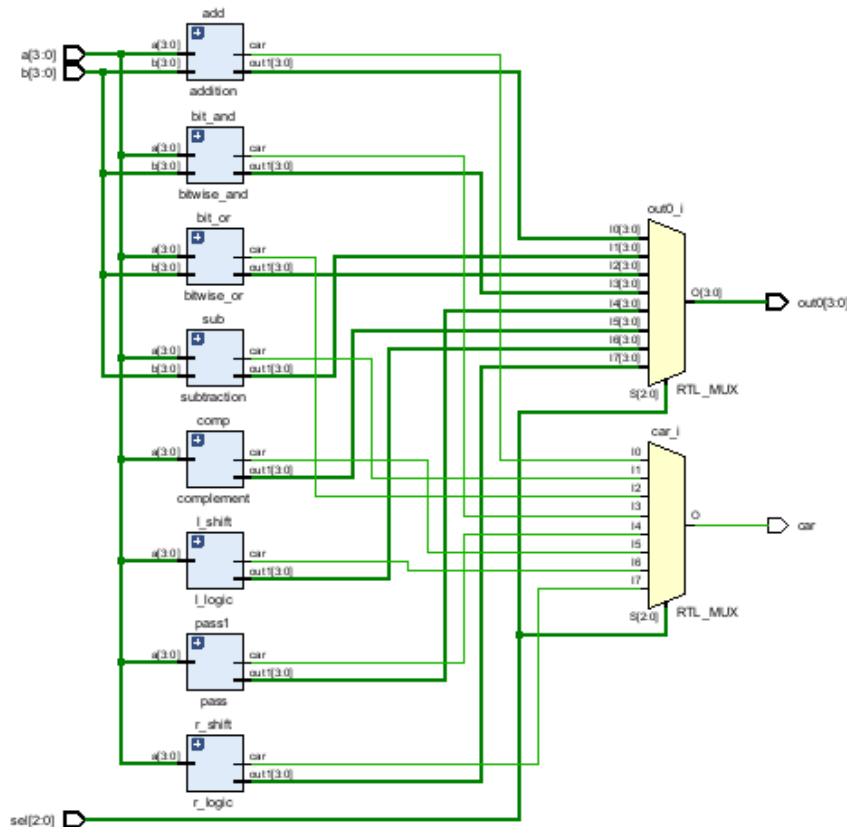


Figure.1 RTL Schematic of the Arithmetic Logic Unit (ALU)

 **Addition:** This function adds two signed 4-bit inputs together. When **sel** is “000”, this operation becomes active.



The diagram illustrates the RTL schematic of a 4-bit subtractor. It features four 1-bit Full Adders (fa1, fa2, fa3, fa4) and an RTL\_INV block. The inputs are a[3:0] and b[3:0]. The output is car[3:0]. The schematic shows the internal logic of the subtractor, including the carry-in and carry-out signals for each adder.

**Bitwise OR-gate:** When sel is “010”, this operation becomes active.



**Bitwise AND-gate:** When **sel** is “011”, this operation becomes active.

 


Figure.5 Bitwise AND-Gate

**Pass Through:** **a** appears unmodified at the output. When **sel** is “100”, this operation becomes active.

 


Figure.6 Pass Through

**Ones' Complement:** All bits of **a** becomes inverted at the output. When **sel** is “101”, this operation becomes active.

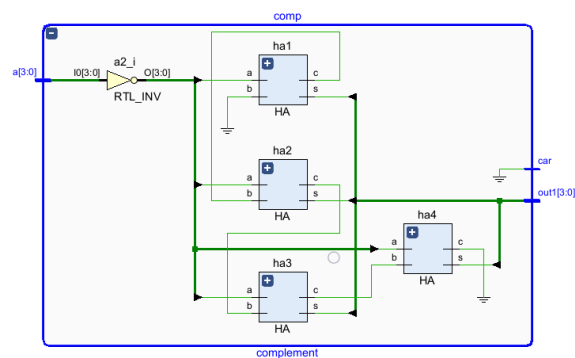


Figure.7 Ones' Complement

**Left Logic Shift:** Moves each bit to one left bit and fills the space with “0”. When **sel** is “110”, this operation becomes active.

 


Figure.8 Left Logic Shift

**Right Logic Shift:** Moves each bit to one right bit and fills the space with “0”. When **sel** is “111”, this operation becomes active.

 


Figure.9 Right Logic Shift

## Results:

Two different waveforms are observed by using two different test benches. The switches and LEDs on BASYS3 is chosen as:

**a** : V17, V16, W16, W17

**b** : V15, W14, W13, V2

**sel** : T2, R3, W2

**out0** : U16, E19, U19, V19

**car** : U15

The waveforms and the BASYS3 representation are in parallel.

 


Figure.10 Left logic shift

sel : 110  
a : 0010  
out0 : 0100

 


Figure.11 Right logic shift

sel : 111  
a : 0100  
out0 : 0010



 


Figure.12 Ones' complement

sel : 101  
a : 0101  
out0 : 1010

 


Figure.13 Pass through

sel : 100  
a : 0101  
out0 : 0101

 


Figure.14 Bitwise AND-gate

sel : 011  
a : 0101  
b : 0111  
out0 : 0101

 


Figure.15 Addition

sel : 000  
a : 0010  
b : 0011  
out0 : 0101

 


Figure.16 Bitwise OR-gate

sel : 010  
a : 0000  
b : 0101  
out0 : 0101



 


Figure.17 Subtraction

sel : 001  
a : 0011  
b : 0001  
out0 : 0010

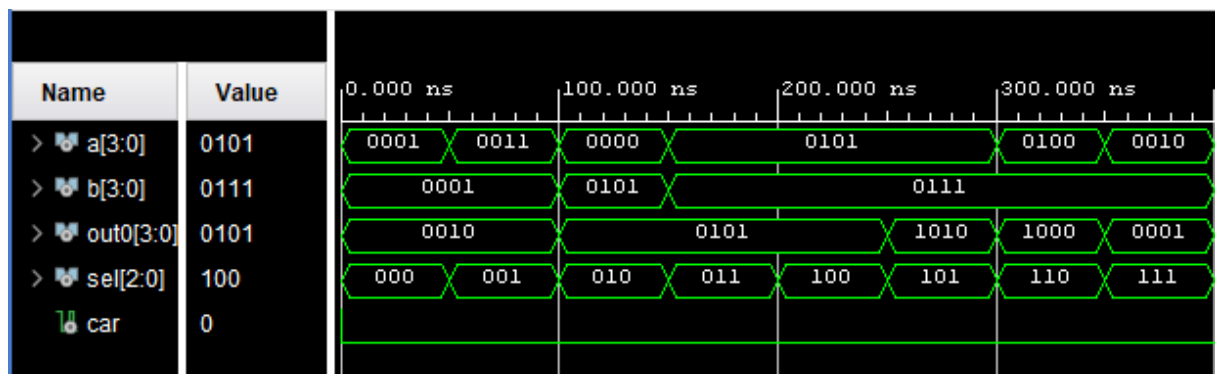


Figure.18 Waveform 1, generated by the first test bench

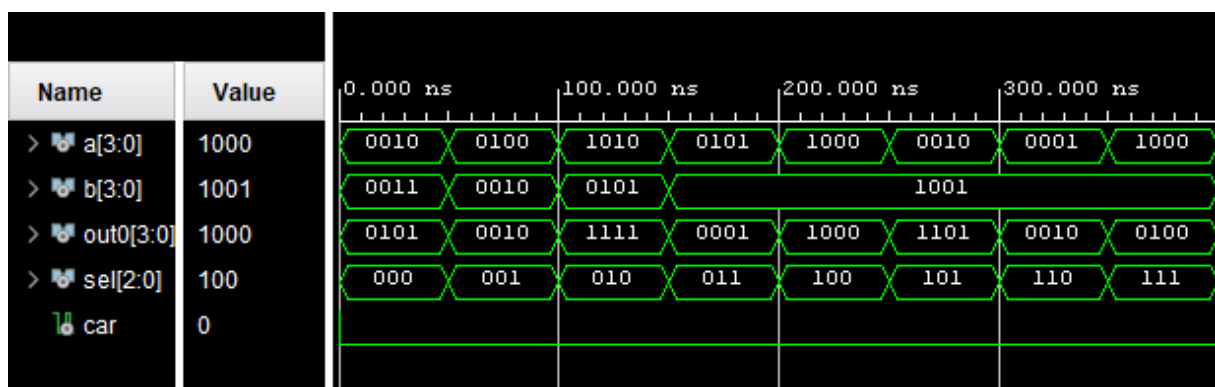


Figure.19 Waveform 2, generated by the second test bench



## Conclusion:

In this lab, we learned how to design an arithmetic logic unit (ALU) capable of performing at least eight different operations including addition, subtraction, one bitwise and one shift operation by using VHDL. The selected operations are: addition, subtraction, bitwise OR-gate, bitwise AND-gate, pass through, ones' complement, left logical shift and right logical shift. A half-adder and a full-adder is created to use in the addition and subtraction operations. Main module `alu.vhd` has the other operations in a modular fashion. 2 different 4-bit signed numbers, **a** and **b**, 3-bit select option **sel**, 4-bit output **out0** and a carry **car** are used in the operations. I learned how to properly implement an ALU in real life. All in all, the experiment was successful at the end.

## APPENDIX

### addition.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity addition is
    Port ( a : in STD_LOGIC_VECTOR(3 downto 0);
          b : in STD_LOGIC_VECTOR(3 downto 0);
          out1 : out STD_LOGIC_VECTOR(3 downto 0);
          car : out STD_LOGIC);
end addition;

architecture add_arch of addition is
    component fa is
        port(a, b, c_in : in std_logic;
             s, c_out : out std_logic);
    end component;

    component ha is
        port(a, b : in std_logic;
             s, c : out std_logic);
    end component;

    signal c : std_logic_vector(3 downto 0);

begin
    ha1 : ha port map (a => a(0), b => b(0), c => c(0), s => out1(0));
    fa1 : fa port map (a => a(1), b => b(1), c_in => c(0), c_out => c(1), s => out1(1));
    fa2 : fa port map (a => a(2), b => b(2), c_in => c(1), c_out => c(2), s => out1(2));
    fa3 : fa port map (a => a(3), b => b(3), c_in => c(2), c_out => c(3), s => out1(3));
    car <= c(2) xor c(3);
end add_arch;
```

## **subtraction.vhd**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity subtraction is
    Port ( a : in STD_LOGIC_VECTOR(3 downto 0);
          b : in STD_LOGIC_VECTOR(3 downto 0);
          out1 : out STD_LOGIC_VECTOR(3 downto 0);
          car : out STD_LOGIC);
end subtraction;

architecture sub_arch of subtraction is
    signal b2 : std_logic_vector(3 downto 0);
    signal c : std_logic_vector(3 downto 0);
    component fa is
        port(a, b, c_in : in std_logic;
             s, c_out : out std_logic);
    end component;
begin
    b2 <= not b;

    fa1: FA port map (a => a(0), b => b2(0), c_in => '1' , s => out1(0), c_out => c(0) );
    fa2: FA port map (a => a(1), b => b2(1), c_in => c(0) , s => out1(1), c_out => c(1) );
    fa3: FA port map (a => a(2), b => b2(2), c_in => c(1) , s => out1(2), c_out => c(2) );
    fa4: FA port map (a => a(3), b => b2(3), c_in => c(2) , s => out1(3), c_out => c(3) );
    car <= c(2) xor c(3);
end sub_arch;
```

## **bitwise\_or.vhd**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity bitwise_or is
    Port (a,b : in std_logic_vector(3 downto 0);
          out1 : out std_logic_vector(3 downto 0);
          car : out std_logic);
end bitwise_or;
architecture Behavioral of bitwise_or is
begin
    out1 <= a or b;
    car <= '0';
end Behavioral;
```



## **bitwise\_and.vhd**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity bitwise_and is
    Port (a,b : in std_logic_vector(3 downto 0);
          out1 : out std_logic_vector(3 downto 0);
          car : out std_logic);
end bitwise_and;
architecture Behavioral of bitwise_and is
begin
    out1 <= a and b;
    car <= '0';
end Behavioral;
```

## **pass.vhd**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity pass is
    Port (a : in std_logic_vector(3 downto 0);
          out1 : out std_logic_vector(3 downto 0);
          car : out std_logic);
end pass ;

architecture Behavioral of pass is
begin
    out1 <= a;
    car <= '0';
end Behavioral;
```

## **complement.vhd**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity complement is
    Port ( a : in STD_LOGIC_VECTOR(3 downto 0);
          out1 : out STD_LOGIC_VECTOR(3 downto 0);
          car : out STD_LOGIC);
end complement;

architecture comp_arch of complement is
    component ha is
        port(a, b : in std_logic;
             s, c : out std_logic);
    end component;

    signal c,a2 : std_logic_vector(3 downto 0);
begin
    a2 <= not a;

    ha1: HA port map (a => a2(0) , b => '0' , c => c(0) , s => out1(0));
    ha2: HA port map (a => a2(1) , b => c(0) , c => c(1) , s => out1(1));
    ha3: HA port map (a => a2(2) , b => c(1) , c => c(2) , s => out1(2));
    ha4: HA port map (a => a2(3) , b => c(2) , c => c(3) , s => out1(3));

    car <= c(3);

    car <= '0';
end comp_arch;
```

## **l\_logic\_shift.vhd**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity l_logic is
    Port (a : in std_logic_vector(3 downto 0);
          out1 : out std_logic_vector(3 downto 0);
          car : out std_logic);
end l_logic;
architecture l_log_arch of l_logic is
begin
    out1 <= a(2 downto 0) & '0';
    car <= '0';
end l_log_arch;
```



## **r\_logic\_shift.vhd**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity r_logic is
    Port (a : in std_logic_vector(3 downto 0);
          out1 : out std_logic_vector(3 downto 0);
          car : out std_logic);
end r_logic;
architecture r_log_arch of r_logic is
begin
    out1 <= '0' & a(3 downto 1);
    car <= '0';
end r_log_arch;
```

## **testbench.vhd**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity testbench is
end testbench;
architecture Behavioral of testbench is
component ALU is
    Port ( a : in STD_LOGIC_VECTOR(3 downto 0);
          b : in STD_LOGIC_VECTOR(3 downto 0);
          sel : in STD_LOGIC_VECTOR(2 downto 0);
          out0 : out STD_LOGIC_VECTOR(3 downto 0);
          car : out STD_LOGIC);
end component;
signal a, b, out0 : std_logic_vector(3 downto 0);
signal sel : std_logic_vector(2 downto 0);
signal car : std_logic;
begin
aluu : ALU
port map(a => a , b => b , out0 => out0 , sel => sel, car => car);
testbench : process
begin
    sel <= "000"; -- add
    a <= "0101";
    b <= "0001";
    wait for 50ns; -- sub
    sel <= "001";
    a <= "0011";
    b <= "0001";
    wait for 50ns; -- bit_or
```

```
sel <= "010";
a <= "0000";
b <= "0101";
wait for 50ns; -- bit_and
sel <= "011";
a <= "0101";
b <= "0111";
wait for 50ns; -- pass1
sel <= "100";
a <= "0101";
wait for 50ns; -- comp
sel <= "101";
a <= "0101";
wait for 50ns; -- l-shift
sel <= "110";
a <= "0100";
wait for 50ns; -- r-shift
sel <= "111";
a <= "0010";
wait for 50ns;
end Behavioral;
```

## **alu.vhd**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity ALU is
    Port ( a : in STD_LOGIC_VECTOR(3 downto 0);
          b : in STD_LOGIC_VECTOR(3 downto 0);
          sel : in STD_LOGIC_VECTOR(2 downto 0);
          out0 : out STD_LOGIC_VECTOR(3 downto 0);
          car : out STD_LOGIC);
end ALU;

architecture ALU_arch of ALU is
    component addition is
        Port ( a : in STD_LOGIC_VECTOR(3 downto 0);
              b : in STD_LOGIC_VECTOR(3 downto 0);
              out1 : out STD_LOGIC_VECTOR(3 downto 0);
              car : out STD_LOGIC);
    end component;

    component subtraction is
        Port ( a : in STD_LOGIC_VECTOR(3 downto 0);
              b : in STD_LOGIC_VECTOR(3 downto 0);
              out1 : out STD_LOGIC_VECTOR(3 downto 0);
              car : out STD_LOGIC);
    end component;

    component bitwise_or is
        Port (a,b : in std_logic_vector(3 downto 0);
              out1 : out std_logic_vector(3 downto 0);
              car : out std_logic);
    end component;

    component bitwise_and is
```



```
Port (a,b : in std_logic_vector(3 downto 0);
```

```
    out1 : out std_logic_vector(3 downto 0);
```

```
    car : out std_logic);
```

```
end component;
```

component pass is

```
Port (a : in std_logic_vector(3 downto 0);
```

```
    out1 : out std_logic_vector(3 downto 0);
```

```
    car : out std_logic);
```

```
end component;
```

component complement is

```
Port ( a : in STD_LOGIC_VECTOR(3 downto 0);
```

```
    out1 : out STD_LOGIC_VECTOR(3 downto 0);
```

```
    car : out STD_LOGIC);
```

```
end component;
```

component l\_logic is

```
Port (a : in std_logic_vector(3 downto 0);
```

```
    out1 : out std_logic_vector(3 downto 0);
```

```
    car : out std_logic);
```

```
end component;
```

component r\_logic is

```
Port (a : in std_logic_vector(3 downto 0);
```

```
    out1 : out std_logic_vector(3 downto 0);
```

```
    car : out std_logic);
```

```
end component;
```

```
signal out1,out2,out3,out4,out5,out6,out7,out8 : std_logic_vector(3 downto 0);
```

```
signal car1,car2,car3,car4,car5,car6,car7,car8 : std_logic;
```

```
begin
```

```
add : addition port map (a => a,b=> b,car=>car1,out1 => out1);
```

```
sub : subtraction port map (a => a,b=> b,car=>car2,out1 => out2);
```

```
bit_or : bitwise_or port map (a => a,b=> b,car=>car3,out1 => out3);
```

```

bit_and : bitwise_and port map (a => a,b=> b,car=>car4,out1 => out4);
pass1 : pass port map (a => a,car=>car5,out1 => out5);
comp : complement port map (a => a,car=>car6,out1 => out6);
l_shift : l_logic port map (a => a,car=>car7,out1 => out7);
r_shift : r_logic port map (a => a,car=>car8,out1 => out8);

mux_process :
process(out1,out2,out3,out4,out5,out6,out7,out8,car1,car2,car3,car4,car5,car6,car7,car8,sel)
begin
  case sel is
    when "000" =>
      out0 <= out1;
      car <= car1;
    when "001" =>
      out0 <= out2;
      car <= car2;
    when "010" =>
      out0 <= out3;
      car <= car3;
    when "011" =>
      out0 <= out4;
      car <= car4;
    when "100" =>
      out0 <= out5;
      car <= car5;
    when "101" =>
      out0 <= out6;
      car <= car6;
    when "110" =>
      out0 <= out7;
      car <= car7;
    when "111" =>

```

```
        out0 <= out8;
        car <= car8;
    when others =>
        out0 <= out8;
        car <= car8;
    end case;
end process;
end ALU_arch;
```

## **ha.vhd**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity HA is
    Port (a,b : in  std_logic;
          c , s : out std_logic);
end HA;
architecture Behavioral of HA is
begin
    s <= a xor b;
    c <= a and b;
end Behavioral;
```

## **fa.vhd**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity FA is
    port(a, b, c_in : in std_logic;
          s, c_out : out std_logic);
end FA;
architecture Behavioral of FA is
begin
    s <= a xor b xor c_in;
    c_out <= ( (a xor b) and c_in ) or (a and b);
end Behavioral;
```

## **const.xdc**

```
set_property PACKAGE_PIN V17 [get_ports {a[0]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {a}]
set_property PACKAGE_PIN V16 [get_ports {a[1]}]
set_property PACKAGE_PIN W16 [get_ports {a[2]}]
set_property PACKAGE_PIN W17 [get_ports {a[3]}]

set_property PACKAGE_PIN V15 [get_ports {b[0]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {b}]
set_property PACKAGE_PIN W14 [get_ports {b[1]}]
set_property PACKAGE_PIN W13 [get_ports {b[2]}]
set_property PACKAGE_PIN V2 [get_ports {b[3]}]

set_property PACKAGE_PIN T2 [get_ports {sel[0]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {sel}]
set_property PACKAGE_PIN R3 [get_ports {sel[1]}]
set_property PACKAGE_PIN W2 [get_ports {sel[2]}]

set_property PACKAGE_PIN U16 [get_ports {out0[0]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {out0}]
set_property PACKAGE_PIN E19 [get_ports {out0[1]}]
set_property PACKAGE_PIN U19 [get_ports {out0[2]}]
set_property PACKAGE_PIN V19 [get_ports {out0[3]}]

set_property PACKAGE_PIN U15 [get_ports {car}]
    set_property IOSTANDARD LVCMOS33 [get_ports {car}]
```