

clock is used to obtain the new clock frequency of the BASYS3 after lowering the internal clock frequency from 100 MHz. This process is made by using *if-elsif-else* statements and *rising_edge* function.

one_second_enable signal and **counter** signal are used to count the passing seconds.

A decoder is written by using *case-when* statements to choose which cathode pattern will be used.

refresh signal is used to generate the 10.5 ms period.

In the 4-to-1 multiplexer, we generate signals based on the 2 most significant digits of the **refresh** signal, which will in turn decide which digits will be displayed. **num_out** signal counts in hexadecimal and is shown in the seven-segment display according to this 4-to-1 multiplexer. **leds** signal attain its value by the 4-bit parts of **num_out** signal.

Results:

A waveform is observed by a test bench (testbench.vhd). also, it should be noted that since our counter changes its value once for every second, we cannot observe the shift in the **display** output in the test bench shown below. This is due to the test bench having a much shorter time span (1000 ns) compared to 1 s. To check, I made the simulation run for 5 s and it worked the way it should but the graph was compressed and looked like a solid green bar. For this purpose, the 5 s test bench result is not included.

The middle button (U18) is used to reset the counter and restart the counting process.

The waveform and the BASYS3 representations are in parallel.

 


Figure.2 Waveform, generated by the test bench

 


Figure.3 Display after 97 seconds (61 in hexadecimal)

 


Figure.4 “Reset” button U18

 


Figure.5 Display after 3549 seconds (DDD in hexadecimal)

Conclusion:

In this lab, we learned how to use the seven-segment display on our BASYS3s by using VHDL. To do that, a second counter in hexadecimal base is implemented. I learned how to properly use the seven-segment display. Every seven-segment display has 4 anodes which controls the digits. Those anodes are chosen by a multiplexer. All in all, the experiment was successful at the end.

APPENDIX

testbench.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std;
entity testbench is
end entity testbench;
architecture Behavioral of testbench is
    signal clock, reset: std_logic := '0';
    signal anode_tb: std_logic_vector(3 downto 0) := (others => '0');
    signal display_tb: std_logic_vector(6 downto 0) := (others => '0');
    component seven_segment_display
        Port (clock, reset: in std_logic := '0';
              anode: out std_logic_vector(3 downto 0);
              display: out std_logic_vector(6 downto 0));
    end component;
begin
    uut: seven_segment_display
    port map ( clock => clock, reset => reset, anode => anode_tb, display => display_tb);
    process
    begin
        clock <= '1';
        wait for 5 ns;
        clock <= '0';
        wait for 5 ns;
    end process;
    process
    begin
```

```
    reset <= '1';  
    wait for 5 ns;  
    reset <= '0';  
    wait;  
    wait for 5 ns;  
    reset <= '1';  
    wait;  
end process;  
end Behavioral;
```

seven_segment_display.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.std_logic_unsigned.all;
entity seven_segment_display is
    Port ( clock , reset : in STD_LOGIC;
          anode : out STD_LOGIC_VECTOR (3 downto 0);
          display : out STD_LOGIC_VECTOR (6 downto 0));
end seven_segment_display;
architecture Behavioral of seven_segment_display is
    signal counter: STD_LOGIC_VECTOR (27 downto 0);
    signal one_second_enable: std_logic;
    signal num_out: STD_LOGIC_VECTOR (15 downto 0);
    signal leds: STD_LOGIC_VECTOR (3 downto 0);
    signal refresh: STD_LOGIC_VECTOR (19 downto 0);
begin
    process(leds)
    begin
        case leds is
            when "0000" => display <= "0000001"; -- "0"
            when "0001" => display <= "1001111"; -- "1"
            when "0010" => display <= "0010010"; -- "2"
            when "0011" => display <= "0000110"; -- "3"
            when "0100" => display <= "1001100"; -- "4"
            when "0101" => display <= "0100100"; -- "5"
            when "0110" => display <= "0100000"; -- "6"
            when "0111" => display <= "0001111"; -- "7"
            when "1000" => display <= "0000000"; -- "8"
            when "1001" => display <= "0000100"; -- "9"
```

```

    when "1010" => display <= "0000010"; -- a
    when "1011" => display <= "1100000"; -- b
    when "1100" => display <= "0110001"; -- C
    when "1101" => display <= "1000010"; -- d
    when "1110" => display <= "0110000"; -- E
    when others => display <= "0111000"; -- F
end case;
end process;
process(clock,reset)
begin
    if reset='1' then
        refresh <= (others => '0');
    elsif rising_edge(clock) then
        refresh <= refresh + 1;
    end if;
    case refresh(19 downto 18) is
        when "00" => anode <= "0111";
            leds <= num_out(15 downto 12);
        when "01" => anode <= "1011";
            leds <= num_out(11 downto 8);
        when "10" => anode <= "1101";
            leds <= num_out(7 downto 4);
        when others => anode <= "1110";
            leds <= num_out(3 downto 0);
    end case;
end process;
process(clock, reset)
begin
    if reset='1' then
        counter <= (others => '0');

```



```

    elsif rising_edge(clock) then
        if counter >= x"5F5E0FF" then
            counter <= (others => '0');
        else
            counter <= counter + "0000001";
        end if;
    end if;
end process;
one_second_enable <= '1' when counter=x"5F5E0FF" else '0';
process(clock, reset)
begin
    if reset='1' then
        num_out <= (others => '0');
    elsif rising_edge(clock) then
        if one_second_enable='1' then
            num_out <= num_out + x"0001";
        end if;
    end if;
end process;
end Behavioral;

```

const.xdc

```
set_property PACKAGE_PIN W5 [get_ports clock]
    set_property IOSTANDARD LVCMOS33 [get_ports clock]
set_property PACKAGE_PIN U18 [get_ports reset]
    set_property IOSTANDARD LVCMOS33 [get_ports reset]

set_property PACKAGE_PIN W7 [get_ports {display[6]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {display[6]}]
set_property PACKAGE_PIN W6 [get_ports {display[5]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {display[5]}]
set_property PACKAGE_PIN U8 [get_ports {display[4]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {display[4]}]
set_property PACKAGE_PIN V8 [get_ports {display[3]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {display[3]}]
set_property PACKAGE_PIN U5 [get_ports {display[2]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {display[2]}]
set_property PACKAGE_PIN V5 [get_ports {display[1]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {display[1]}]
set_property PACKAGE_PIN U7 [get_ports {display[0]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {display[0]}]

set_property PACKAGE_PIN U2 [get_ports {anode[0]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {anode[0]}]
set_property PACKAGE_PIN U4 [get_ports {anode[1]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {anode[1]}]
set_property PACKAGE_PIN V4 [get_ports {anode[2]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {anode[2]}]
set_property PACKAGE_PIN W4 [get_ports {anode[3]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {anode[3]}]
```